

Design and Implementation of an LED Chaser Circuit Using NE555 Timer and CD4017 Counter

Department of Electronics and Communication Engineering (ECE)

Date: 25 May 2026

1. Introduction

The objective of this mini-project is to design and implement an LED Chaser Circuit using a NE555 Timer IC and CD4017 Decade Counter IC. The circuit produces a sequential lighting effect in which LEDs turn ON and OFF one after another, creating a running or chasing light pattern.

LED chaser circuits are widely used in decorative lighting systems, advertisement displays, emergency warning indicators, and digital display applications. The project demonstrates the practical implementation of pulse generation, clock signal propagation, and sequential digital logic operations.

The NE555 timer is configured in astable mode to generate continuous clock pulses. These pulses are supplied to the CD4017 decade counter, which activates its output pins sequentially. Each output drives an LED, producing the chasing effect.

This project provides a strong understanding of:

- Pulse generation using timer circuits.
- Sequential logic operations.
- Clock pulse propagation.
- Practical implementation of digital electronics.
- LED interfacing and current limiting techniques.

By constructing the hardware physically, the project bridges theoretical concepts of electronics with real-time circuit implementation.

2. Working Principle and Theoretical Context

2.1 Pulse Generation Using NE555 Timer

The NE555 Timer IC operates in astable multivibrator mode to generate a continuous square wave output. The frequency of oscillation depends on the resistor and capacitor values connected externally.

The generated clock pulses are continuously fed to the clock input pin of the CD4017 counter IC.

Astable Frequency Equation

The oscillation frequency of the NE555 timer is given by:

$$f = 1.44 / ((R1 + 2R2) \times C)$$

Where:

- R1 and R2 are timing resistors.
- C is the timing capacitor.
- f is the output frequency.

The output pulse rate determines the speed of the LED chasing effect.

2.2 Sequential Operation of CD4017 Counter

The CD4017 is a CMOS decade counter with ten decoded outputs. On every incoming clock pulse:

- Only one output becomes HIGH at a time.
- The HIGH state shifts sequentially from Q0 to Q9.
- After Q9, the sequence resets back to Q0.

Each output is connected to an LED through a current-limiting resistor. As the outputs change sequentially, the LEDs glow one after another, creating the running light effect.

This operation demonstrates the principle of sequential digital logic and clock-driven state transitions.

3. Circuit Architecture & Signal Flow

3.1 Block Diagram Description

The LED chaser circuit consists of the following major blocks:

1. Power Supply Section
2. NE555 Timer Pulse Generator
3. CD4017 Decade Counter
4. LED Output Section

Signal Flow:

- The 3.7V power supply energizes the complete circuit.
- The NE555 timer generates periodic clock pulses.
- Clock pulses are supplied to the CD4017 counter.
- The CD4017 activates outputs sequentially.

- LEDs connected to the outputs glow in sequence.

3.2 Timing and Signal Integrity

The timing capacitor and resistors determine the pulse frequency. Stable timing components are necessary to maintain smooth LED transitions.

The current-limiting resistors protect the LEDs from excessive current flow and improve operational reliability.

Proper grounding and secure breadboard connections help avoid signal noise and irregular LED operation.

3.3 Reset Mechanism

The reset pin of the CD4017 can be connected strategically to limit the number of active LEDs in the sequence.

For example:

- Connecting reset to Q5 creates a 5-LED chaser.
- Leaving reset disconnected allows full 10-LED operation.

This provides flexibility in designing customized lighting patterns.

4. Components Used

Component	Specification	Purpose
NE555 Timer IC	DIP-8 Timer IC	Generates clock pulses in astable mode
CD4017 IC	CMOS Decade Counter	Activates outputs sequentially
LEDs	5mm Standard LEDs	Visual indication of running sequence
Resistors	680Ω	Limits LED current
Timing Resistors	1kΩ	Controls pulse frequency
Capacitor	10μF, 0.01μ	Determines oscillation timing
Breadboard	Standard	Circuit assembly
Jumper Wires	Connecting Wires	Electrical interconnections
Power Supply	3.7V DC	Powers the circuit

5. Results

The implemented LED chaser circuit successfully generated sequential blinking of LEDs using clock pulses from the NE555 timer and output sequencing from the CD4017 counter.

The LEDs turned ON one after another in a cyclic manner, demonstrating proper operation of the timer and counter stages.

Observed Performance

Clock Pulse Active Output LED Status

1st Pulse	Q0	LED1 ON
2nd Pulse	Q1	LED2 ON
3rd Pulse	Q2	LED3 ON
4th Pulse	Q3	LED4 ON
5th Pulse	Q4	LED5 ON
6th Pulse	Q5	LED6 ON
7th Pulse	Q6	LED7 ON
8th Pulse	Q7	LED8 ON
9th Pulse	Q8	LED9 ON
10th Pulse	Q9	LED10 ON

The speed of the LED chasing pattern was successfully varied by changing the timing resistor and capacitor values.

The hardware testing confirmed:

- Stable pulse generation by the NE555 timer.
- Correct sequential counting by the CD4017.
- Smooth LED chasing effect.
- Reliable operation under 3.7V DC supply.

6. Applications

The LED chaser circuit has several practical applications in electronics and lighting systems:

1. **Decorative Lighting Systems**
Used in festivals, homes, and event lighting for attractive running light patterns.
 2. **Advertisement Displays**
Used in sign boards and commercial displays to attract attention.
 3. **Emergency Warning Indicators**
Sequential flashing lights are used in safety and alert systems.
 4. **Automotive Lighting**
Implemented in modern vehicle indicator systems and decorative lighting.
 5. **Educational Demonstration**
Helps students understand timer circuits, counters, and sequential digital logic.
 6. **Sequential Control Systems**
Used in automation systems requiring ordered activation of outputs.
-

7. Conclusion

The LED chaser mini-project was successfully designed and implemented using the NE555 Timer IC and CD4017 Decade Counter IC. The project demonstrated the practical application of pulse generation, clock-driven sequencing, and digital output control.

The circuit operated reliably and produced a smooth sequential lighting pattern. The project provided valuable hands-on experience in circuit design, breadboard implementation, timing analysis, and digital electronics concepts.

This mini-project serves as an effective educational experiment for understanding sequential logic systems and real-world electronic circuit applications.